


2-Stage OTA

Specifications:-

DC Gain $> 60\text{dB}$
GBW $= 5\text{MHz}$
Process $= 180\text{nm}$
 $\text{PM} \geq 60^\circ$
Slew Rate $\geq 10\text{V}/\mu\text{sec}$
 $\text{ICMR}(+) = 1.6\text{V}$
 $\text{ICMR}(-) = 0.8\text{V}$

$C_L = 10\text{pF}$
 $V_{DD} = 1.8\text{V}$
 $\mu_n C_{ox} = 246.74\text{ }\mu\text{A}/\text{V}^2$
 $\mu_p C_{ox} = 92.75\text{ }\mu\text{A}/\text{V}^2$

Circuit diagram:-

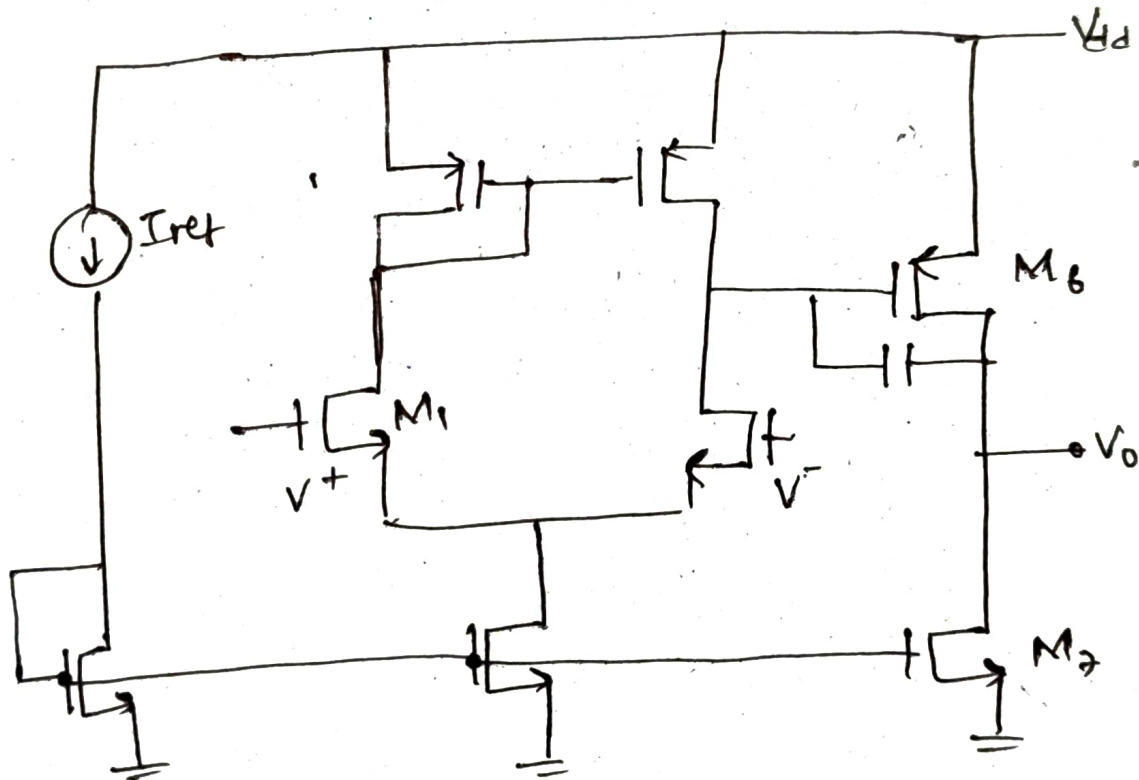

Method of Design:-

- $\frac{W}{L}$ of M_3, M_4 is found using $\text{ICMR}(+)$
- $\frac{W}{L}$ of M_1, M_2 is found using GBW
- I_S is found using slew rate
- $\frac{W}{L}$ of M_5 found using $\text{ICMR}(-)$

→ $\frac{W}{L}$ of M_6 using phase margin and zero location

→ $\frac{W}{L}$ of M_2 by M_5 (related)

→ C_c using C_L and phase margin.

Calculations:-

① For $PM > 60^\circ$: $C_c \geq 0.22 C_L$

$$\text{As: } \phi_M = 60^\circ = 180^\circ - \tan^{-1}\left(\frac{\omega}{|P_1|}\right) - \tan^{-1}\left(\frac{\omega}{|P_2|}\right) - \tan^{-1}\left(\frac{\omega}{z_1}\right)$$

② GBW (Since $GBW = \text{Open loop UGF}$) ($f=1$)

$$120^\circ = \tan^{-1}\left(\frac{GB}{|P_1|}\right) + \tan^{-1}\left(\frac{GB}{|P_2|}\right) + \tan^{-1}\left(\frac{GB}{z_1}\right)$$

$$= \tan^{-1}(\text{DC gain}) + \tan^{-1}\left(\frac{GB}{|P_2|}\right) + \tan^{-1}(0.1)$$

[$z_1 = 10GB$]

$$A_V(0) \rightarrow \infty$$

$$24.3^\circ = \tan^{-1}\left(\frac{GB}{|P_2|}\right)$$

$$|P_2| \geq 2.2 GB$$

$$(z_1 \geq 10GB) \quad \frac{g_{m6}}{C_c} \geq 10 \frac{g_{m2}}{C_c} \Rightarrow g_{m6} \geq 10 g_{m2}$$

$$\frac{g_{m6}}{C_2} \geq 2.2 \frac{g_{m2}}{C_c} \Rightarrow C_c \geq 0.22 C_L$$

$$\rightarrow C_L = 10 pF$$

$$C_c \geq 2.2 pF$$

$$\text{Let } \boxed{C_c = 3 pF}$$

② I_S : Slew rate = $\frac{I_S}{C_c}$

$$I_S = 10 \text{ V}/\mu\text{s} \times 3 \text{ pF} = 30 \mu\text{A}$$

③ M_1 & M_2

$$g_{m1} = \text{GBW} \cdot C_c \cdot 2\lambda = 94.24 \mu\text{S}$$

$$\left(\frac{W}{L}\right)_1 = \frac{g_{m1}^2}{\mu_n C_{ox} \times 2 I_D} = \frac{(94.24 \mu)^2}{246.79 \times 30 \times 10^{-6}} = 1.2$$

④ M_3 & M_4

$$\left(\frac{W}{L}\right)_{3,4} = \frac{2 I_{D3}}{\mu_p C_{ox} \left[V_{DD} - I_{CMR}(\pm) - V_{t3 \max} + V_{t1 \min} \right]^2}$$

$$V_{t3 \max} = 0.433 \text{ V}$$

$$V_{t1 \min} = 0.31 \text{ V}$$

$$\left(\frac{W}{L}\right)_3 = \frac{30}{92.75 (1.8 - 1.6 - 0.43 + 0.31)^2} = 54.55 \approx 55$$

$$\left(\frac{W}{L}\right)_{3,4} = 55$$

⑤ For M_5, M_8

$$V_{dsat5} = ICMR(-) - V$$

$$\text{Since } ICMR(+) = V_{DD} - \sqrt{\frac{I_5}{\beta_3}} - V_{to3max} + V_{tmin}$$

$$\text{as } ICMR(+) - V_{tmin} < V_{G3}$$

$$V_{G3} = V_{DD} - V_{ov3} - V_{tp}$$

⑤ For M_5 & M_8

$$V_{dsat5} = ICMR(-) - V_{S5} - \sqrt{\frac{I_5}{\beta_1}} - V_{th1max}$$

$$\text{Since } ICMR(-) - V_{ov1} - V_{th1max} = V_{dsat5}$$

$$V_{dsat5} = 0.8 - 0 - 0.319 - 0.38 = 0.1V$$

$$\left(\frac{W}{L}\right)_5 = \frac{2I_5}{\mu_n C_{ox} (V_{dsat5})^2} = \frac{2 \times 30}{246.94 \times 0.1^2} = 24.31$$

$$\left(\frac{W}{L}\right)_{5,8} = 24$$

⑥ For M_6

$$g_{m6} = 10g_{m1} = 942.4 \mu$$

$$g_{m4}^2 = 2I_4 \mu_p C_{ox} \times \left(\frac{W}{L}\right)_4 \Rightarrow g_{m4} = \sqrt{30 \times 92.97 \times 55}$$

$$g_{m4} = 391.20 \mu$$

$$\left(\frac{W}{L}\right)_6 = \frac{g_{m6} \times \left(\frac{W}{L}\right)_4}{g_{m4}}$$

[Since M_4 & M_6 have equal overdrive]

$$= 132.49 \approx 132$$

⑦ For MA:

$$I_6 = \frac{\left(\frac{W}{L}\right)_6 \times I_4}{\left(\frac{W}{L}\right)_4} = \frac{132 \times 15 \mu}{55} = 36 \mu A$$

$$\left(\frac{W}{L}\right)_7 = \frac{I_7 \times \left(\frac{W}{L}\right)_5}{I_5} = 28$$

Here for no systematic offset:

$$2 \times \frac{\left(\frac{W}{L}\right)_7}{\left(\frac{W}{L}\right)_5} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} \quad \text{is satisfied}$$

Data:

$$I_{dc} = 30 \mu A \quad C_c = 3 pF \quad C_L = 10 pF \quad \text{Let } L = 500 nm$$

$$M_{1,2} \quad W = 600 nm \quad L = 500 nm$$

$$M_{3,4} \quad W = 27 \mu m \quad L = 500 nm$$

$$M_5 \quad W = 12 \mu m \quad L = 500 nm$$

$$M_6 \quad W = 66 \mu m \quad L = 500 nm$$

$$M_7 \quad W = 14 \mu m \quad L = 500 nm$$

$$M_8 \quad W = 12 \mu m \quad L = 500 nm$$

Analysis:

Total Open loop gain : $65 dB \geq 60 dB$

GBW = 3 dB of closed loop : $5.07 MHz$

Phase margin = 63°

Phase margin was expected to be 60° .